

## RLC

$$\frac{d^2V_C(t)}{dt^2} + 2\alpha \frac{dV_C(t)}{dt} + \omega_0^2 V_C(t) = 0$$

$$s^2 e^{st} + 2\alpha s e^{st} + \omega_0^2 e^{st} \quad s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\beta = \frac{\alpha}{\omega_0}$$

$$Q = \sqrt{\frac{L}{CR^2}}$$

$$V_C(t) = K_1 e^{(-\alpha + \sqrt{\alpha^2 - \omega_0^2})t} + K_2 e^{(-\alpha - \sqrt{\alpha^2 - \omega_0^2})t}$$

find later

$$K_1 + K_2 = V_{00}$$

$$K_1 S_1 + K_2 S_2 = 0$$

$$K_1 \frac{s_1 - s_2}{s_1 + s_2} = V_{00}$$

$$K_2 = \frac{s_1 - s_2}{s_1 + s_2} V_{00}$$

$$K_1 = \frac{s_1 + s_2}{s_1 + s_2} V_{00}$$

$$\text{if } \beta > 1 \text{ (overdamped): } K_1 e^{s_1 t} + K_2 e^{s_2 t}$$

$$\text{if } \beta < 1 \text{ (underdamped): } K_1 e^{-\alpha t} \cos(\omega_0 t) + K_2 e^{-\alpha t} \sin(\omega_0 t)$$

$$\text{if } \beta = 1 \text{ (critically damped): } K_1 e^{-\alpha t} + K_2 t e^{-\alpha t} \quad (s_1 = s_2)$$

$$V_{00} e^{-\alpha t} (\cos(\omega_0 t) + \frac{\alpha}{\omega_0} \sin(\omega_0 t)) \quad V_{00} (e^{-\alpha t} - \frac{\alpha}{\omega_0} t e^{-\alpha t})$$

## Phasors

### Time Domain

$$V(t) = V_0 \cos(\omega t + \theta) \quad (\text{voltage})$$

$$i(t) = i_0 \cos(\omega t + \phi) \quad (\text{current})$$

$$L \text{ (inductors)} \quad Z_L = j\omega L$$

$$C \text{ (capacitors)} \quad Z_C = \frac{1}{j\omega C}$$

$$R \text{ (resistors)} \quad Z_R = R$$

$$\cos(x - \frac{\pi}{2}) = \sin(x) \quad v(t) = V_0 \sin(\omega t + \phi) \Rightarrow \tilde{v} = \frac{V_0 e^{j\theta}}{i}$$

### Phasor Domain

$$\tilde{V} = V_0 e^{j\theta}$$

$$\tilde{i} = i_0 e^{j\phi}$$

$$\omega = \text{frequency}$$

$$\tilde{V}_1 = |V| e^{j\theta}$$

$$\tilde{V}_2 = |V| |V_2| e^{j(\theta - \omega t)}$$

$$\tilde{V}_1 = \frac{|V|}{|V_2|} e^{j(\theta - \phi)}$$

$$\tilde{V}_2 = \frac{|V|}{|V_1|} e^{j(\theta - \theta)}$$

$$\tilde{V}_1 = \frac{|V|}{|V_2|} e^{j(\theta - \phi)}$$

## Filters

### low pass

$$H(j\omega) = \frac{1}{1 + j\frac{\omega}{\omega_c}}$$

for an AC component:

$$\frac{1}{1 + j\frac{\omega}{\omega_c}} \approx 1 \quad \omega \ll \omega_c$$

$$\omega_c = \frac{1}{RC}$$

### high pass

$$H(j\omega) = \frac{j\frac{\omega}{\omega_c}}{1 + j\frac{\omega}{\omega_c}}$$

for an AC component:

$$\frac{j\frac{\omega}{\omega_c}}{1 + j\frac{\omega}{\omega_c}} \approx 1 \quad \omega \gg \omega_c$$

$$\omega_c = \frac{1}{RC}$$

### band pass

$$P_1 \quad \frac{1}{C_1} \quad \frac{1}{C_2} \quad \frac{1}{R_1} \quad \frac{1}{R_2}$$

$$C_1 \quad \frac{1}{C_2} \quad \frac{1}{R_1} \quad \frac{1}{R_2}$$

$$C_2 \quad \frac{1}{C_1} \quad \frac{1}{R_1} \quad \frac{1}{R_2}$$

$$R_1 \quad \frac{1}{C_1} \quad \frac{1}{C_2} \quad \frac{1}{R_2}$$

$$R_2 \quad \frac{1}{C_1} \quad \frac{1}{C_2} \quad \frac{1}{R_1}$$

$$\text{good for } \left[ \frac{1}{R_2 C_2}, \frac{1}{R_1 C_1} \right]$$

### Notch Filter

### opposite of band pass

$$H = 0 \text{ at}$$

$$\omega = \frac{1}{RC}$$

$$H = \frac{j\omega + \frac{1}{RC}}{j\omega + \frac{1}{RC} + j\omega - \frac{1}{RC}}$$

$$= \frac{1}{1 + j\frac{\omega}{\omega_c} + j\frac{\omega}{\omega_c} - j\frac{1}{\omega_c}}$$

### Poles / Zeros

$$H(j\omega) = K \frac{(j\omega)^N (1 + j\frac{\omega}{\omega_p})(1 + j\frac{\omega}{\omega_n})}{(j\omega)^M (1 + j\frac{\omega}{\omega_z})(1 + j\frac{\omega}{\omega_n})}$$

$$\text{poles}$$

$$\text{zeros}$$

## Capacitors

$$C = \frac{Q}{V} \quad V = \frac{Q}{C} \quad Q = CV \quad C = \frac{\epsilon_0 A}{d}$$

$$i = C \frac{dV}{dt} \quad \frac{dV(t)}{dt} = -\frac{1}{RC} V(t) \quad P = \frac{1}{2} QV$$

$$\text{discharging: } V(t) = V_0 e^{-\frac{t}{RC}}$$

$$\text{charging: } V(t) = V_{DD} (1 - e^{-\frac{t}{RC}})$$

$$T = RC$$

## Inductors

$$L = \frac{N^2 \mu A}{l}$$

$$N \text{ turns}$$

$$l_1, l_2$$

$$i_1, i_2$$

$$V_1, V_2$$

$$V_1, V_2$$

$$i(t) = I_0 e^{-\frac{t}{L}}$$

$$(inductor + current source)$$

$$V(t) = L \frac{di(t)}{dt}$$

$$E = \frac{1}{2} L i^2$$


$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$V_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

$$V_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$V_2 = -M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

## Current Divider

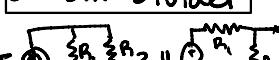

$$I_S = \frac{U_1}{R_1 + R_2}$$

$$U_{out} = \frac{R_2}{R_1 + R_2} U_1$$

## RLC (Phasors)


$$\text{In series: } \omega_0 = \frac{1}{\sqrt{LC}} \quad Q = \frac{\omega_0 L}{R} = \frac{1}{R\sqrt{LC}}$$

$$\text{In parallel: } \omega_0 = \frac{1}{\sqrt{LC}} \quad Q = \frac{R}{\omega_0 L} = \omega_0 R C = R \sqrt{\frac{C}{L}}$$

## Feedback



$$V_{out} = V_{in}(1 + \frac{R_f}{R})$$

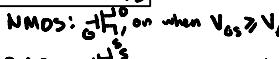

$$V_{out} = -V_{in} \frac{R_f}{R}$$

## Transistors

$$\text{NMOS: } G \overset{\rightarrow}{h_i} \text{ on when } V_{GS} \geq V_{th}$$

$$\text{PMOS: } G \overset{\leftarrow}{h_o} \text{ on when } V_{GS} \leq -|V_{th}|$$

$$\text{inverter: } V_{in} \rightarrow V_{out} \quad (\text{just an RC})$$

$$\text{NMOS: } G \overset{\rightarrow}{h_i} \text{ on when } V_{GS} \geq V_{th}$$

$$\text{PMOS: } G \overset{\leftarrow}{h_o} \text{ on when } V_{GS} \leq -|V_{th}|$$

$$\text{IGNORE THE CAPS!}$$

## Complex Numbers

$$\alpha = x + jy$$

$$\alpha^* = x - jy$$

$$R\{\alpha\} = \frac{1}{2}(\alpha + \alpha^*) = x$$

$$I\{\alpha\} = \frac{1}{2}(\alpha - \alpha^*) = y$$

$$\alpha\alpha^* = |\alpha|^2 = |x|^2 + |y|^2$$

$$\theta = \angle \alpha = \arctan\left(\frac{y}{x}\right)$$

$$\alpha = |\alpha| e^{j\theta} = |\alpha| (\cos(\theta) + j\sin(\theta))$$

$$|e^{j\theta}| = 1$$

$$R\{e^{j\omega t}\} = \cos(\omega t)$$

$$R\{e^{j\omega t - \frac{\pi}{2}}\} = \sin(\omega t)$$

$$\frac{1}{2}(e^{j\omega t} + \bar{e}^{j\omega t}) = \cos(\omega t)$$

## Trig

	$0^\circ$	$30^\circ$	$45^\circ$	$60^\circ$	$90^\circ$
sin	0	$\frac{1}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{\sqrt{3}}{2}$	1
cos	1	$\frac{\sqrt{3}}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{1}{2}$	0
tan	0	$\frac{1}{\sqrt{3}}$	1	$\sqrt{3}$	infinity